

# Lecture 16 – Sequential circuits 2

Dr. Aftab M. Hussain,  
Assistant Professor, PATRIOT Lab, CVEST

## Chapter 5


# Latches

---

- A storage element in a digital circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit), until directed by an input signal to switch states
- Such a storage element is called a latch
- The major differences among various types of storage elements are in the number of inputs they possess and in the manner in which the inputs affect the binary state

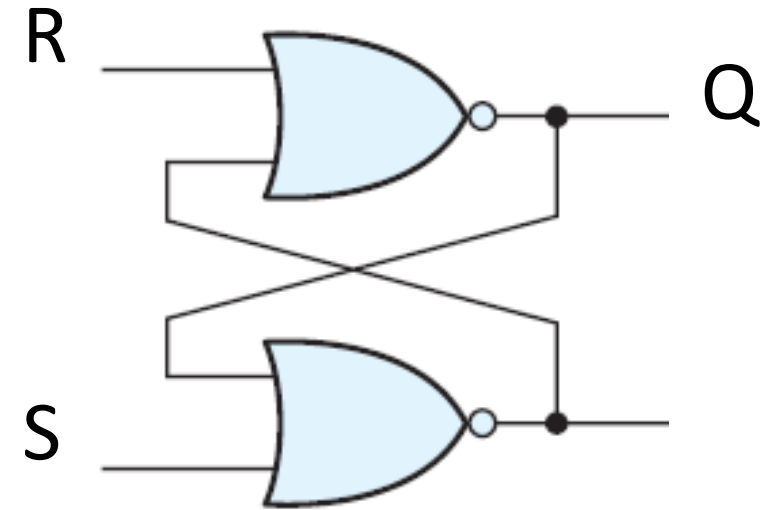
# SR Latch

- The *SR* latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates, and two inputs labeled *S* and *R*
- Let's analyze...



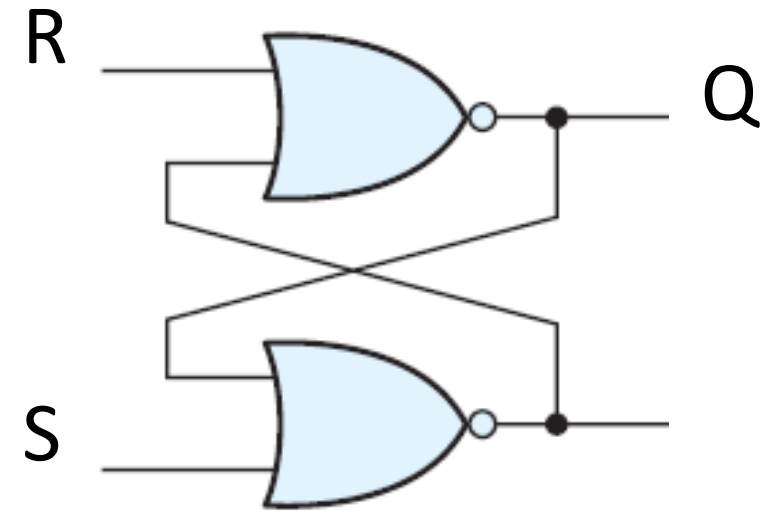
# SR Latch

- We realize that the outputs  $Q$  and  $Q'$  are normally the complement of each other
- The latch has two stable states
- When output  $Q = 1$  and  $Q' = 0$ , the latch is said to be in the *set state*
- When  $Q = 0$  and  $Q' = 1$ , it is in the *reset state*


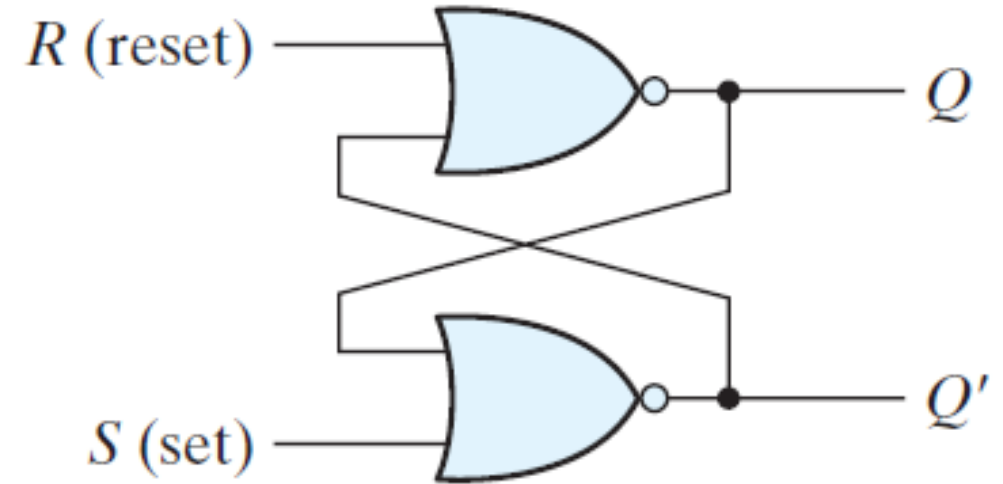
# SR Latch


- Setting and resetting can be done through the two inputs (SR)
- After setting or resetting, applying 00 at the input retains the previous state
- However, when both inputs are equal to 1 at the same time, a condition in which both outputs are equal to 0 (rather than be mutually complementary) occurs
- If both inputs are then switched to 0 simultaneously, the device will enter an unpredictable or undefined state or a metastable state



$S$	$R$	$Q$	$Q'$	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$ )
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$ )
1	1	0	0	(forbidden)
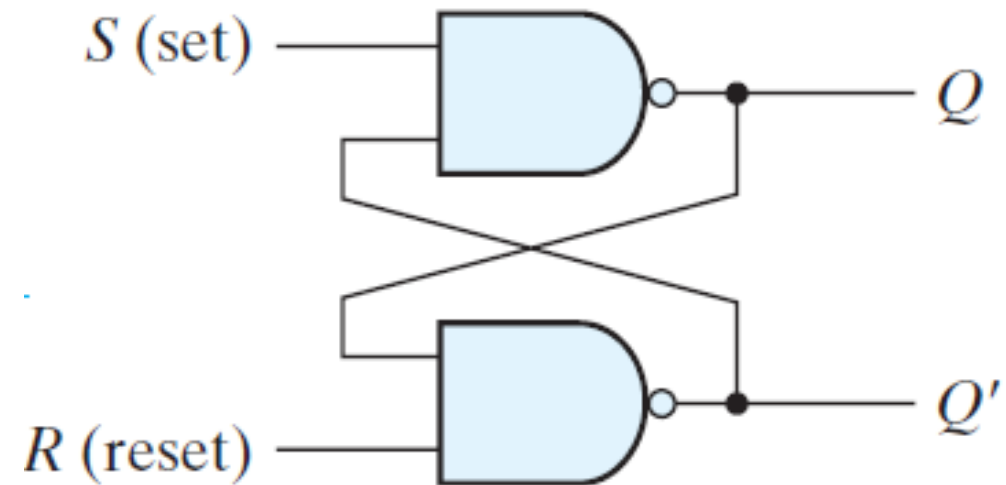
# SR Latch – NAND implementation


- The *SR* latch with two cross-coupled NAND gates behaves in a similar way to NOR implementation
- It operates with both inputs normally at 1, unless the state of the latch has to be changed
- The application of 0 to the *S* input causes output *Q* to go to 1, putting the latch in the set state
- When the *S* input goes back to 1, the circuit remains in the set state
- The condition that is forbidden for the NAND latch is both inputs being equal to 0 at the same time, an input combination that should be avoided



<i>S</i>	<i>R</i>	<i>Q</i>	<i>Q'</i>	
1	0	0	1	
1	1	0	1	(after <i>S</i> = 1, <i>R</i> = 0)
0	1	1	0	
1	1	1	0	(after <i>S</i> = 0, <i>R</i> = 1)
0	0	1	1	(forbidden)
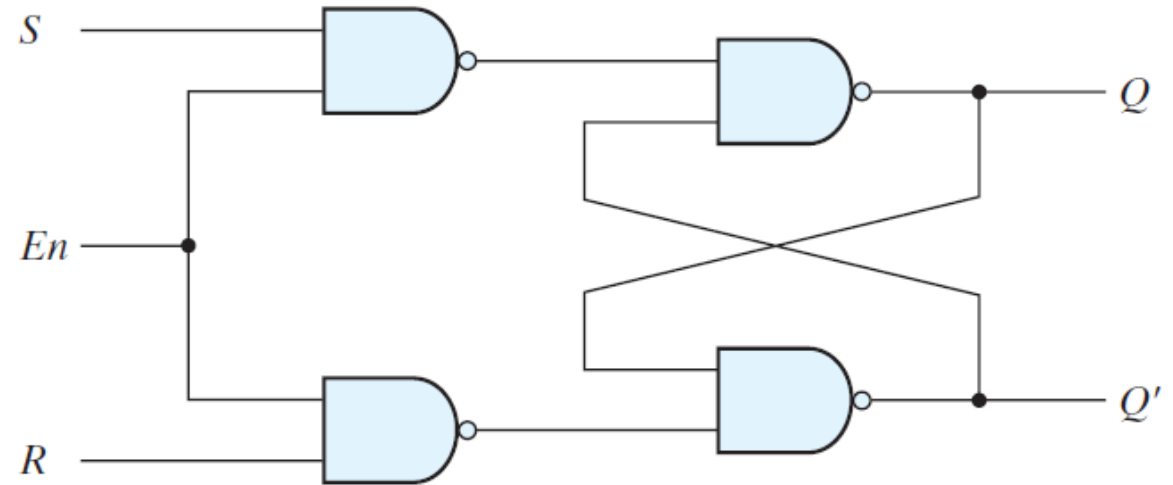
# Latch with enable


- The operation of the basic *SR* latch can be modified by providing an additional input signal that determines (controls) *when* the state of the latch can be changed by determining whether *S* and *R* (or *S* and *R*) can affect the circuit
- It consists of the basic *SR* latch and two additional NAND gates
- The control input *En* acts as an *enable* signal for the other two inputs
- The outputs of the NAND gates stay at the logic-1 level as long as the enable signal remains at 0
- This is the quiescent condition for the *SR* latch



<i>En</i>	<i>S</i>	<i>R</i>	Next state of <i>Q</i>
0	X	X	No change
1	0	0	No change
1	0	1	<i>Q</i> = 0; reset state
1	1	0	<i>Q</i> = 1; set state
1	1	1	Indeterminate
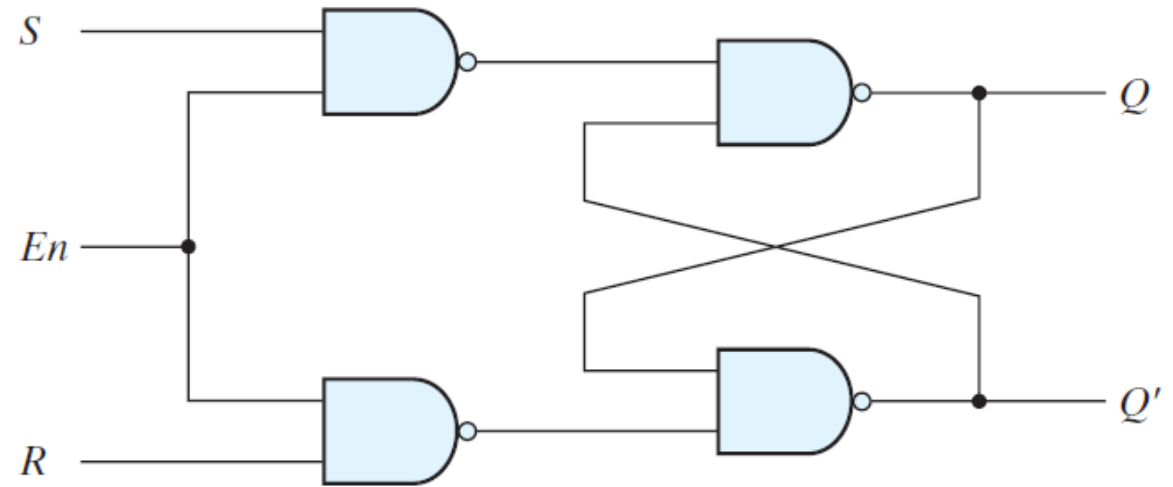
# Latch with enable

- When the enable input goes to 1, information from the  $S$  or  $R$  input is allowed to affect the latch
- The set state is reached with  $S = 1$ ,  $R = 0$ , and  $En = 1$  (active-high enabled) and reset is reached with  $S = 0$ ,  $R = 1$ , and  $En = 1$
- In either case, when  $En$  returns to 0, the circuit remains in its previous stable state
- Further, when  $En = 1$  and both the  $S$  and  $R$  inputs are equal to 0, the state of the circuit does not change




$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate


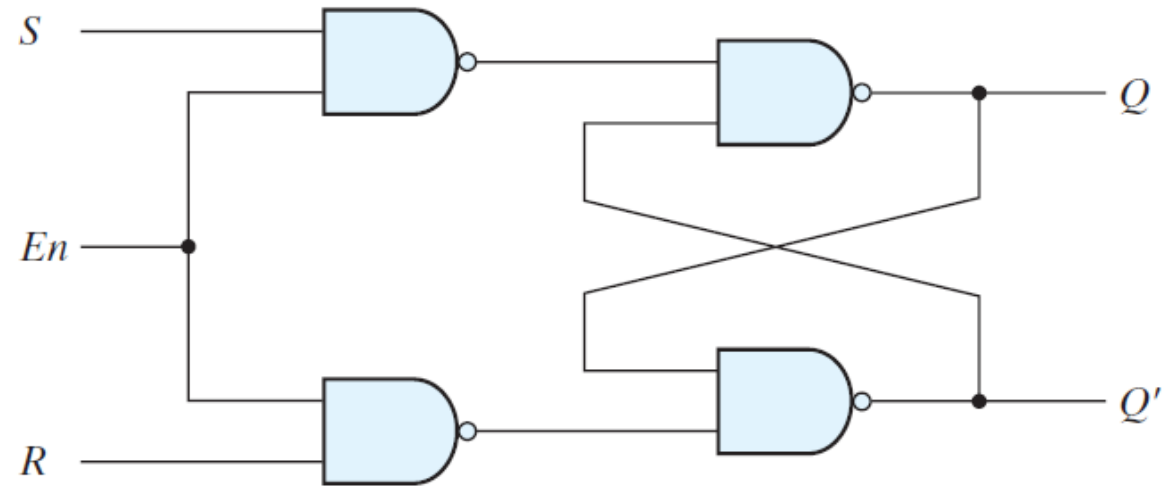
# Latch with enable


- An indeterminate condition occurs when all three inputs are equal to 1
- This condition places 0's on both inputs of the basic  $SR$  latch, which puts it in the undefined state
- When the enable input goes back to 0, one cannot conclusively determine the next state, because it depends on whether the  $S$  or  $R$  input goes to 0 first
- This indeterminate condition makes this circuit difficult to manage, and it is seldom used in practice
- Nevertheless, the  $SR$  latch is an important circuit because flip-flops are constructed from it



$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate
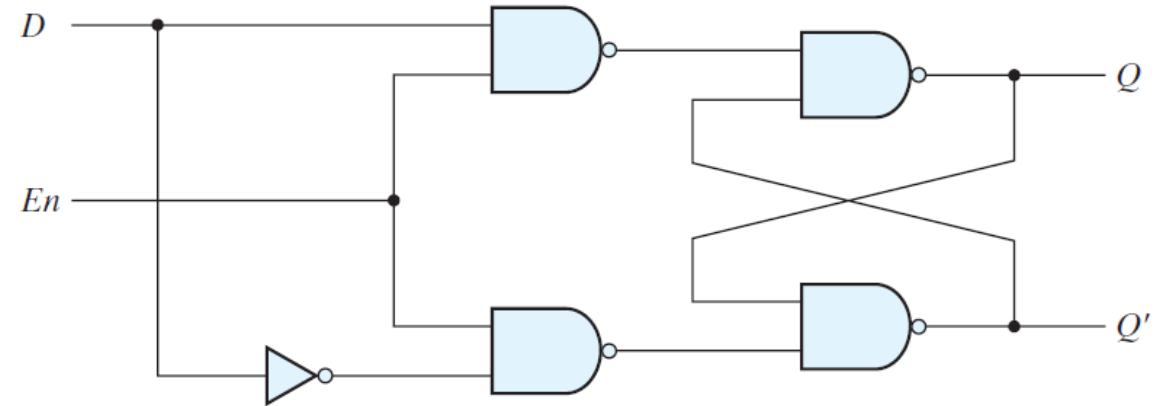
# D Latch


- One way to eliminate the undesirable condition of the indeterminate state in the  $SR$  latch is to ensure that inputs  $S$  and  $R$  are never equal to 1 at the same time
- This is done in the  $D$  latch
- The  $D$  input goes directly to the  $S$  input, and its complement is applied to the  $R$  input
- As long as the enable input is at 0, the cross-coupled  $SR$  latch has both inputs at the 1 level and the circuit cannot change state regardless of the value of  $D$
- The  $D$  input is sampled when  $En = 1$ . If  $D = 1$ , the  $Q$  output goes to 1, placing the circuit in the set state
- If  $D = 0$ , output  $Q$  goes to 0, placing the circuit in the reset state



$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state
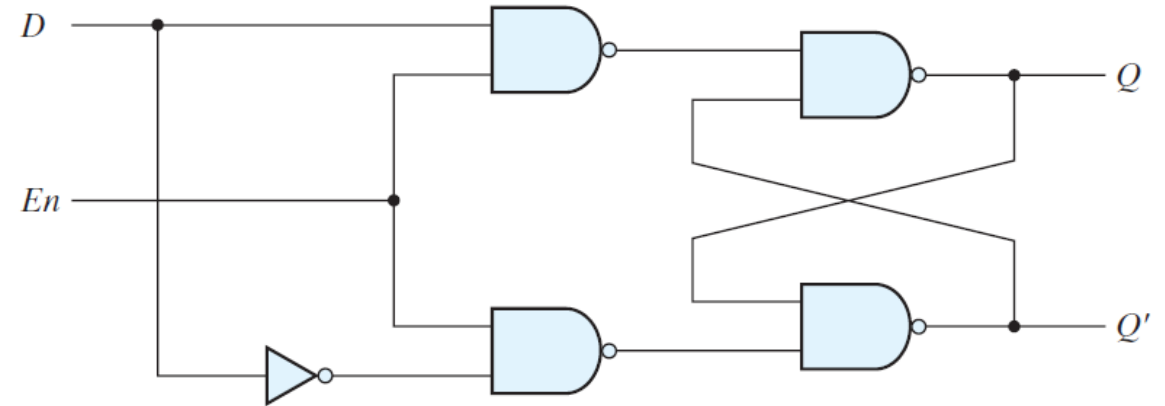
# D Latch


- The  $D$  latch receives that designation from its ability to hold *data* in its internal storage
- It is suited for use as a temporary storage for binary information between a unit and its environment
- The binary information present at the data input of the  $D$  latch is transferred to the  $Q$  output when the enable input is asserted
- The output follows changes in the data input as long as the enable input is asserted
- This situation provides a path from input  $D$  to the output, and for this reason, the circuit is often called a *transparent* latch



$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state
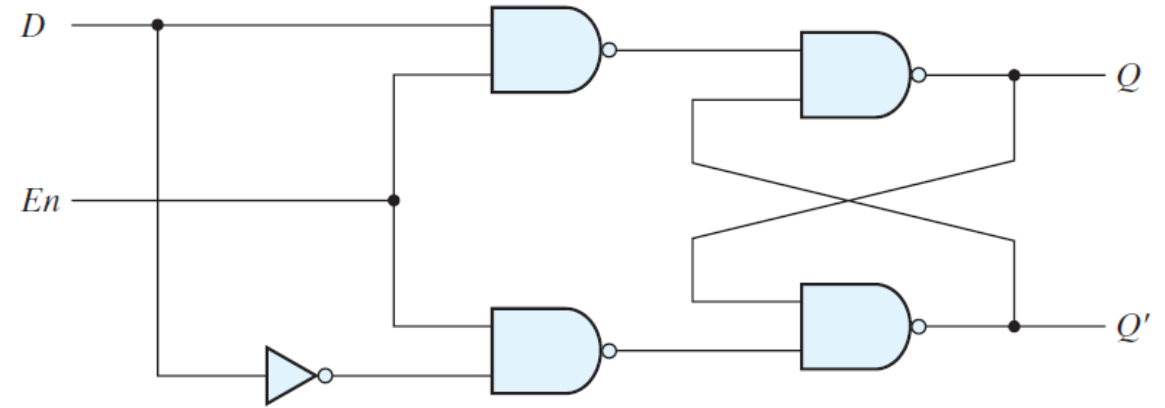
# D Latch

- When the enable input signal is de-asserted, the binary information that was present at the data input at the time the transition occurred is retained (i.e., stored) at the  $Q$  output until the enable input is asserted again
- Note that an inverter could be placed at the enable input
- Then, depending on the physical circuit, the external enabling signal will be a value of 0 (active low) or 1 (active high)



$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state