

**NAME : MALLA SAILESH**  
**ROLL NUMBER : 2021101106**  
**GROUP NUMBER : 6**

**LAB 7**  
**DIGITAL SYSTEMS AND MICROCONTROLLERS**


**AIM :**

- To implement and verify the operation of the binary cell of RAM based on RS FlipFlop as stated later .

**ELECTRONIC COMPONENTS :**

- Arduino
- Breadboard
- NOR Gate , 3 input AND Gate , NOT Gate
- LED , Resistor

**REFERENCE CIRCUIT :**

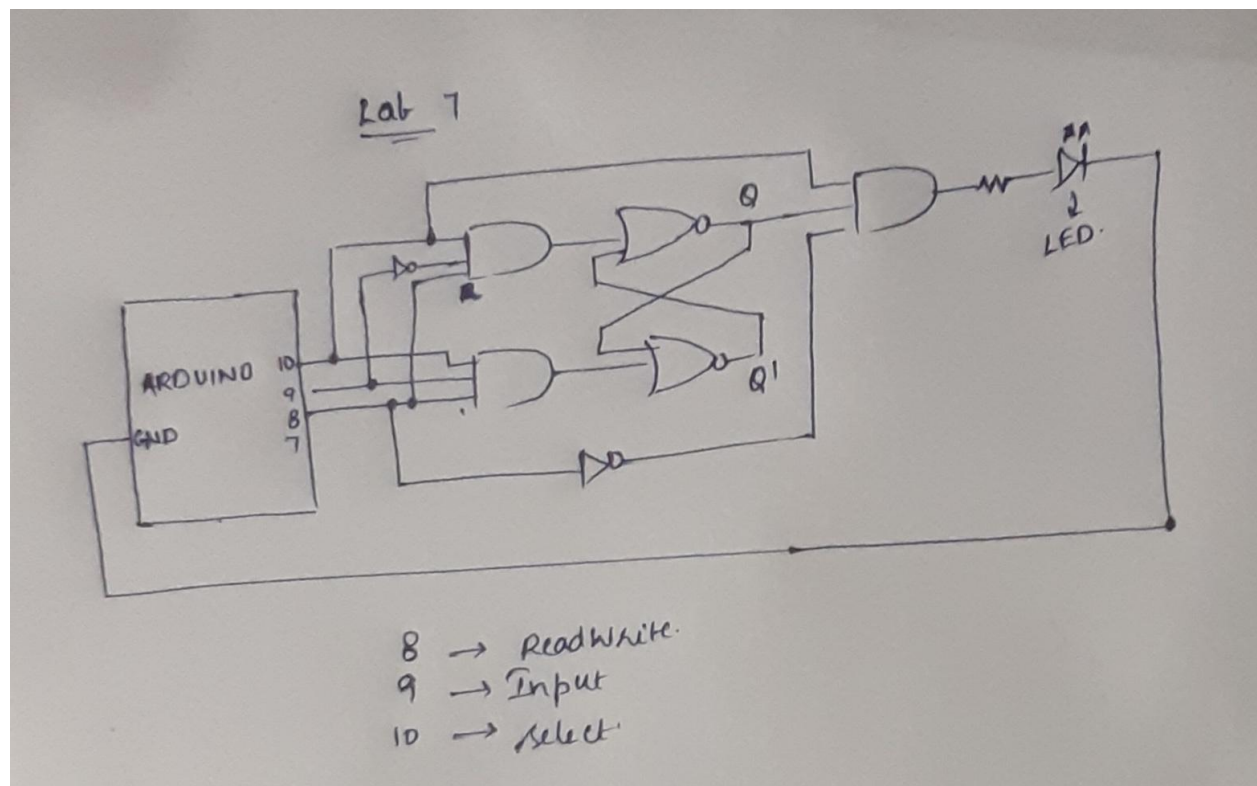

**PROCEDURE :**

- The cell has 3 inputs and 1 output . 3 inputs are ReadWrite , Input , Select .
- The Select input is used to access the cell either for reading or writing .
- ReadWrite -> 1 signifies the Write operation and ReadWrite -> 0 signifies the Read operation.
- If the Select input is 1 and ReadWrite is 1 then the value placed into the cell only depends on the input i.e if input is 1 then the value stored in the cell is 1 , if the input is 0 then the value stored in the cell is 0. In this case the output will be zero.

- If the Select input is 1 and ReadWrite is 0 then value stored in the cell is given as output thus reading the value inside the cell .In this case the cell does not take any inputs from any input . So output is the value which is previously stored in the cell . If initially the stored value in the cell is 1 then the output will be 1 else the output is 0.
- Code :

```
int select = 8;
int input = 9;
int readwrite = 10;
void setup()
{
  pinMode(8,OUTPUT);
  pinMode(9,OUTPUT);
  pinMode(10,OUTPUT);
  Serial.begin(9600);//sets the data rate to 9600 bps
}
void loop()
{
  Serial.print("ReadWrite:");
  while(Serial.available()==0){};
  readwrite = Serial.read();
  readwrite = readwrite - '0' ;
  Serial.println(readwrite);
  digitalWrite(10,readwrite);

  Serial.print("input:");
  while(Serial.available()==0){};
  input = Serial.read();
  input = input - '0' ;
  Serial.println(input);
  digitalWrite(9,input);

  Serial.print("select:");
  while(Serial.available()==0){};
  select = Serial.read();
  select = select - '0' ;
  Serial.println(select);
  digitalWrite(8,select);
}
```

### **OBSERVATIONS :**

- When the Select line is 1 and ReadWrite is 1 then the value stored in the cell is only dependent on the input .

- When the select line is 1 and ReadWrite is 0 the the output is only dependent on the value stored in the cell .
- When the select line is 0 , the value of the output of the flipflop (Q) is same as the previous value of Q .But the output will be zero .

**LINK TO TINKERCAD SIMULATION :**

<https://www.tinkercad.com/things/hThxJjHPZEJ-grand-bruticus/editel?sharecode=HYTVnuLRPMHCm6AyEcFW3qpdXHe6HmjVhZecx2IYTtg>